

EMMANUEL L. KOMWEDZAI


N4

287472

1.1.10 v

- 1.1.1 J
- 1.1.2 E
- 1.1.3 A
- 1.1.4 F
- 1.1.5 ~~A~~ B D K
- 1.1.6 B
- 1.1.7 C
- 1.1.8 G
- 1.1.9 ~~A~~ H

1.2

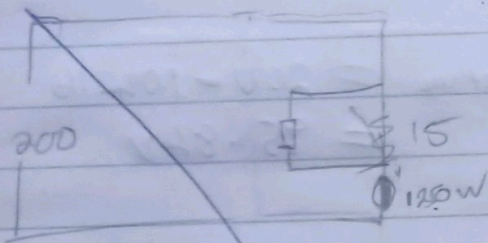

$$I_a = I_L - I_{sh}$$

$$I_{sh} = \frac{V}{R_s}$$

$$P_o = 1250 \quad I_a = 12A$$

$$R_{sc} = 15 \quad V = 200$$

$$R_{he} = \frac{V_{sh}}{I_{sh}}$$

$$P_i = V_i \times I_c$$

$$= 1250 \times 12 \times 200$$

$$= 2400 W$$

$$R_{sc.T} \text{ heater } R:$$

$$P = I^2 R$$

$$\frac{1250 \times 12^2}{12^2}$$

$$R = 8,681$$

$$\text{Total series } R = 15 + 8,681$$

$$= 23,681 \Omega$$

$$V_{sc} = 23,681 \times 12$$



$$\text{Total Rreturn} = 16,67 - 32$$

$$1.2 \quad R_T = \frac{200}{12} \\ = 16,67 \Omega$$

$$\therefore R_H = \frac{V^2}{P} \\ = \frac{200^2}{1250} \\ = 32 \Omega$$

$$R_{\text{rester}} = \frac{1250}{12^2} \\ = 8,68 \Omega$$

$$V_{\text{rester}} = 12 \times 8,68 \\ = 104,16$$

$$\therefore V_{\text{return}} = 200 - 104,16 \\ = 95,84 \text{ V}$$


$$R_{\text{return}} = \frac{95,84}{12} \\ = 7,99 \Omega$$

$$R_{\text{unkno}} = 15 - 7,99 \\ = \underline{\underline{7,01 \Omega}}$$



$$\begin{aligned}
 2.1 \quad \text{MMF} &= R \times \Phi \\
 &= 60000 \times 6 \times 10^{-3} \\
 &= 360 \text{ A}
 \end{aligned}$$

2.2

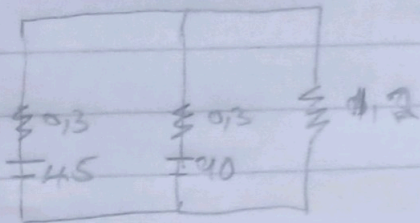

$$I = I_1 + I_2$$

$$E_1 = I_1 r_1 + I R$$

$$E_1 = I_1 r_1 + (I_1 + I_2) R \quad \dots 0$$

$$E_2 = I_2 r_2 + (I_1 + I_2) R \quad \dots 20$$

$$I_1 = \frac{E_1 - I_2 R}{r_1 + R}$$

$$I_2 = \frac{E_2 - I_1 R}{r_2 + R}$$

$$I_1 = \frac{E_1 (r_2 + R) - E_2 R}{r_1 r_2 + (r_1 + r_2) R + R^2}$$

$$\begin{aligned}
 &= \frac{45 (0.3 + 1.2) - 90 (1.2)}{0.3 \times 0.3 (0.3 + 0.3) 1.2 + 1.2^2} \\
 &= -15 \text{ A}
 \end{aligned}$$



$$I_2 = \frac{90(0,3+1,2) - 45 \times 1,2}{0,3 \times 0,3(0,3+0,3) 1,2+1,2^2}$$

$$= 50 \text{ A}$$

$$I_T = 50 + (-15)$$

$$= 35 \text{ A}$$

$$V_{RL} = IR$$

$$35 \times 1,2$$

$$= \underline{\underline{42 \text{ V}}}$$

2.2.2  $I_1 = -15 \text{ A}$

$I_2 = 50 \text{ A}$

2.3 Farad is the SI unit of the capacitance. equal to the capacitance of a capacitor in which one coulomb of charge cause a potential difference of one volt.

~~$$C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

$$= 17$$~~

2.4a)  $V = \frac{Q}{C} = \frac{1750 \times 10^6}{(17+8)}$

$$= \underline{\underline{54 \text{ F}}}$$



$$\begin{aligned} 2.2.2 \quad C_1 &= \frac{Q}{V} \\ &= \frac{1750 \times 10^{-6}}{17} \\ &= 102,94 \mu\text{F} \end{aligned}$$

$$\begin{aligned} C_2 &= \frac{Q}{V} \\ &= \frac{1750 \times 10^{-6}}{8} \\ &= 218,75 \mu\text{F} \end{aligned}$$

$$2.4 \quad R_2 = R_1 [1 + \alpha (T_2 - T_1)]$$


$$\alpha = \frac{\frac{R_2}{R_1} - 1}{T_2 - T_1}$$

$$\alpha = \frac{\frac{234}{210} - 1}{100 - 60}$$

$$\alpha = \underline{\underline{0,002857^\circ\text{C}}}$$



Scale 1cm : 5V  
1cm : 1A

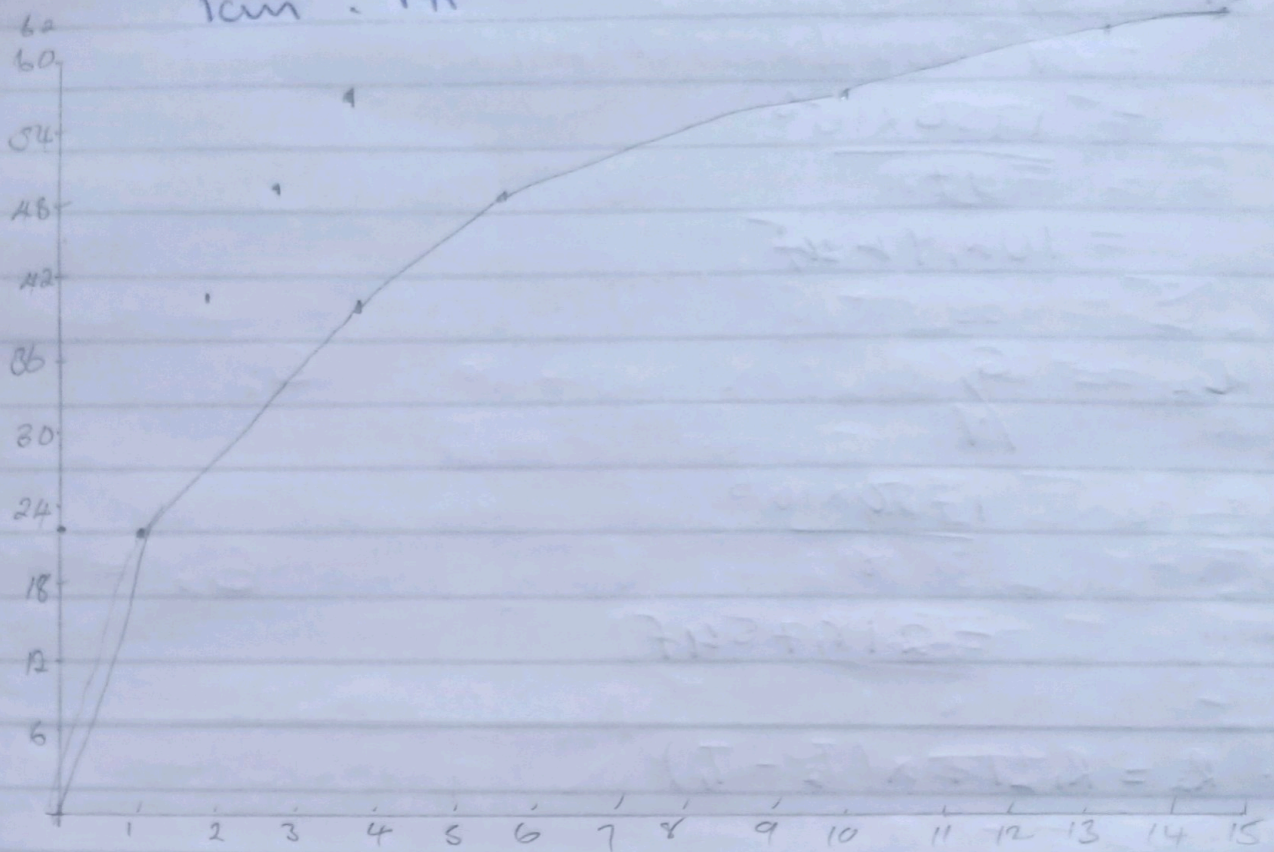

$$I = \frac{V}{R}$$

$$= \frac{V}{5}$$

$$3.3 \quad R_T = R_a + R_s \quad \therefore V_T = 80 \times 0,6$$

$$= 0,4 + 0,2 \quad = 30V$$

$$= 0,6 \Omega$$

$$Emf = V_a - V_{cs}$$

$$= 400 - 30$$

$$= \underline{370V}$$

3.3 use to support the field coils

3.5 commutator ; rotor ; armature coil.



$$T = \frac{1}{f}$$

$$f = \frac{1}{T}$$

$$= \frac{1}{25 \times 10^{-3}}$$

$$= 40 \text{ Hz}$$

4.4

$$Z_1 = 15 + j10$$

$$Z_2 = 15 - j10$$

$$Z_1 = 18,028 \angle 33,690$$

$$Z_2 = 18,028 \angle -33,690$$

$$Z_T = \frac{Z_1 \times Z_2}{Z_1 + Z_2} = \frac{18,028 \angle 33,690 \times 18,028 \angle -33,690}{(15 + j10)(15 - j10)}$$

$$= \frac{325,009 \angle 0}{30}$$

$$= \underline{10,834 \Omega}$$

4.42  $I = \frac{\$ 270,825}{10,834}$

$$I_T = 24,9976$$

$$= 25,00 \text{ A}$$



Chief is the to ~~support~~ support the armature assembly.

$$4.1 \quad E_m = 2\pi BANn$$

$$\therefore B = \frac{V_1}{4.44 \cdot N_1 \cdot f \cdot A}$$

$$= \frac{1110}{4.44 \cdot 50 \cdot 20010 \times 10^{-4}}$$

$$= 2.5 \text{ T}$$

$$4.2 \quad \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{1110}{111} = \frac{200}{N_2}$$

$$N_2 = 111 \times 200$$

$$1110 N_2 = \frac{22200}{110}$$

$$N_2 = 20 \text{ turns}$$

$$4.2 \quad V_{m_x} = V_{r_m} \times \sqrt{2}$$

$$= 422,2 \times \sqrt{2}$$

$$= 599,909 \text{ V}$$

$$= \underline{599,909 \text{ V}}$$



$$421 \quad T = \frac{1}{f}$$

$$f = \frac{1}{T}$$

$$= \frac{1}{25 \times 10^{-3}}$$

$$= 40 \text{ Hz}$$

444

$$Z_1 = 15 + j10$$

$$Z_2 = 15 - j10$$

$$Z_1 = 18,028 \angle 33,690$$

$$Z_2 = 18,028 \angle -33,690$$

$$Z_T = \frac{Z_1 \times Z_2}{Z_1 + Z_2} = \frac{18,028 \angle 33,690 \times 18,028 \angle -33,690}{(15 + j10)(15 - j10)}$$

$$= \frac{325,009 \angle 0}{30}$$

$$= \underline{10,834 \Omega}$$

$$442 \quad I = \frac{\$ 270,825}{10,834}$$

$$I_T = 24,9976$$

$$= 25,00 \text{ A}$$



$$\begin{aligned}
 4.44) \quad P &= VI \\
 &= 270,825 \times 25 \\
 &= \underline{\underline{6770,625 \text{ W}}}
 \end{aligned}$$

$$\begin{aligned}
 5.11 \quad B &= \frac{V_i}{4.44 \times f \times N} \\
 &= \frac{2000}{4.44 \times 50 \times 200} \\
 &= \underline{\underline{0,022 \text{ Wb}}}
 \end{aligned}$$

$$\begin{aligned}
 5.12 \quad P_0 &= 10 \times 0,3 \times 2000 \\
 &= \underline{\underline{600 \text{ W}}}
 \end{aligned}$$

$$\begin{aligned}
 5.13 \quad I_m &= I_0 \times \sin(\cos^{-1} 0,3) \\
 I_m &= 10 \times \sin 72,542 \\
 &= 9,54 \text{ A}
 \end{aligned}$$

5.2 Oil Natural

Oil forced natural

Air forced natural

water forced.